

Lab-02

Name : Ashfia Khanam

ID : 18301231

Sec : CSE-09

Cowise : CSE250


Experiment Name : Introduction to series and parallel circuits.

Experiment name : Introduction to series and parallel circuits.

Objective : The experiment is to acquaint ~~the students~~^{us} with series-parallel circuits and to give them the idea about how to connect different circuits in bread board.

Apparatus : Fig. Figure : 1 : Multimeter Two $10k\Omega$ resistors, two $1k\Omega$ resistors, DC 12V power source, Jumper wires, bread-board.

Circuit Diagram :

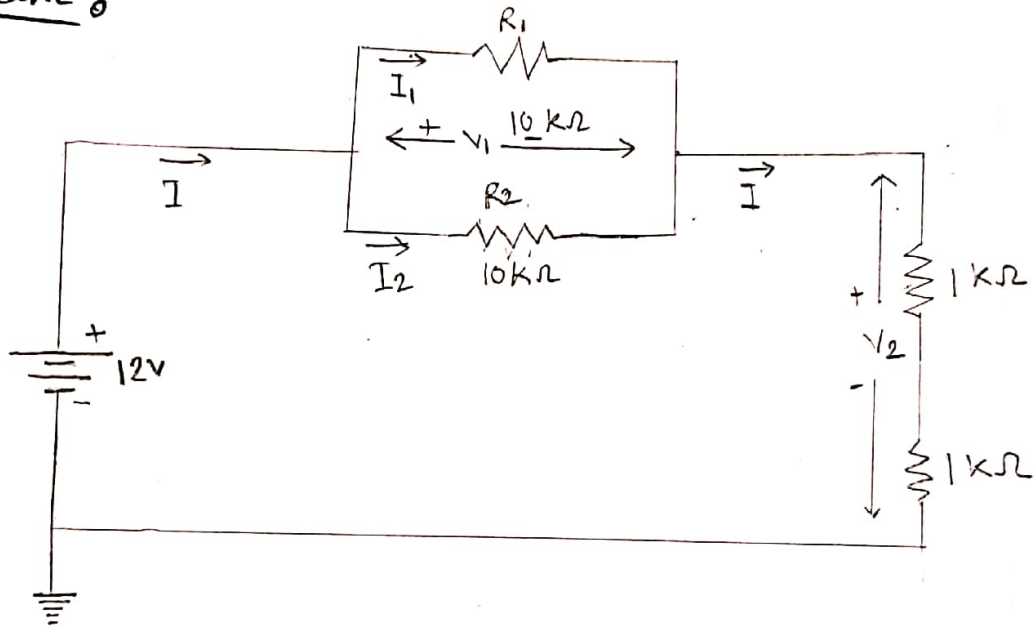

Result/Analysis section :

i) Theoretical calculation : Figure 01 :

$$\begin{aligned} \text{Total resistance of the circuit} &= \left\{ \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} + R_3 + R_4 \right\} k\Omega \\ &= \left(\left(\frac{1}{10} + \frac{1}{10} \right)^{-1} + 1 + 1 \right) k\Omega \\ &= 7 k\Omega \end{aligned}$$

Now, $V = IR$

$$\Rightarrow I = \frac{V}{R} = \frac{12}{7k} A = 0.001714 A = 1.714 \text{ mA}$$

As R_3 and R_4 are in series alignment the current run through them will be 1.714 mA .

Now voltage runs through R_1 and R_2 are,

$$V_1 = I \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \frac{12}{17k} \times 5k = \frac{60}{7} = 8.5714 \text{ volts}$$

Now the current runs through R_1 is,

$$I_1 = \frac{V_1}{R_1} = \frac{60/7}{10k} = 0.85714 \text{ mA}$$

Now the current runs through R_2 is,

$$I_2 = \frac{V_1}{R_2} = \frac{60/7}{10k} = 0.85714 \text{ mA}$$

Thus, the voltage runs through R_3 and R_4 is,

$$\begin{aligned} V_2 &= (I R_3 + I R_4) = \left(\frac{12}{7k} \times 1k \right) + \left(\frac{12}{7k} \times 1k \right) \\ &= 1.712 + 1.712 \text{ volts} \\ &= 3.428 \text{ volts.} \end{aligned}$$

ii) Verification of the results from proteus simulation,
Figure 1:


From the proteus simulation we get,

I	1.71mA	XXXX		Resistance	Voltage	Current
I ₁	0.857mA		R ₁	10k Ω	8.57V	0.857mA
I ₂	0.857mA		R ₂	10k Ω	8.57V	0.857mA
V ₁	8.57V		R ₃	1k Ω	1.71V	1.71mA
V ₂	3.42V		R ₄	1k Ω	1.71V	1.71mA

Apparatus : Figure 2.11

Apparatus: Figure 2: Multimeter, three 10k Ω resistors, three 1k Ω resistors, Jumper wire, bread board, DC 12V power supply.

Circuit Diagram: Figure 2:

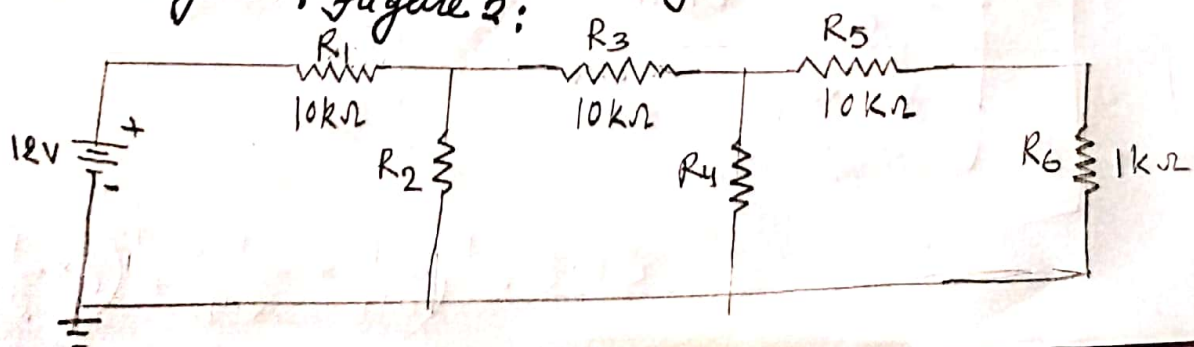

Result/Analysis : i) Theoretical calculation ~~Result~~

Figure 2 :

$$R_{4,5,6} = \left(\frac{1}{R_4} + \frac{1}{R_5 + R_6} \right)^{-1} = \left(\frac{1}{1k} + \frac{1}{11k} \right)^{-1} = \frac{11}{12} k\Omega = 916.667 \Omega$$

$$R_{2,3,4,5,6} = \left(\frac{1}{R_2} + \frac{1}{R_3 + R_{4,5,6}} \right)^{-1} = \left(\frac{1}{1k} + \frac{1}{10k + 916.667} \right)^{-1} = 916.084 \Omega$$

$$\therefore R_{1,2,3,4,5,6} = 10000 + 916.084 \Omega = 10916.084 \Omega$$

$$\therefore I_1 = \frac{V}{R} = \frac{12}{10916.084} = 0.0010993 A = 1.0993 mA$$

Now,

$$V_1 = I R_{1,2,3,4,5,6}$$

$$= 0.0010993 \times 10000 = 10.993 \text{ volts}$$

$$V_2 = I \times R_{2,3,4,5,6}$$

$$= 0.0010993 \times 916.084 = 1.007 \text{ volts}$$

$$\therefore I_2 = \frac{V_2}{R_2} = \frac{1.007}{1000} = 0.001007 A = 1.007 mA$$

$$\therefore I_3 = \frac{V_2}{R_{3,4,5,6}} = \frac{1.007}{10916.667} = 92.244 \times 10^{-6} A$$

$$\therefore V_3 = I_3 R_3 = 92.244 \times 10^{-6} \times 10000 = 0.922 \text{ volts}$$

$$\therefore V_4 = I_3 R_4 = 92.244 \times 10^{-6} \times 916.67 = 0.0845 \text{ volts}$$

$$\therefore I_4 = \frac{V_4}{R_4} = \frac{0.0845}{1000} = 8.45 \times 10^{-5} A$$

$$\therefore I_5 = \frac{V_4}{R_{5,6}} = \frac{0.0845}{11000} = 7.682 \times 10^{-6} A$$

$$\therefore V_5 = I_5 R_5 = 7.682 \times 10^{-6} \times 10000 = 0.0768 \text{ volts}$$

$$\therefore V_6 = I_5 R_6 = 7.682 \times 10^{-6} \times 1000 = 0.00768 V$$

ii) Verification of the results from proteus,

Figure 2: From the proteus file, we get,

V1	10.993
V2	1.00704
V3	0.92247
V4	0.0845
V5	0.7687
V6	0.00768

	Resistance	Current
R1	10k Ω	0.001099
R2	1k Ω	0.0010070
R3	10k Ω	9.224×10^{-5}
R4	1k Ω	8.456×10^{-5}
R5	10k Ω	1.768×10^{-5}
R6	1k Ω	1.760×10^{-6}


Question and Answers :

1) The calculated value of the currents are $I = 1.71 \text{ mA}$;

$$I_1 = 0.85 \text{ mA}; I_2 = 0.857 \text{ mA}.$$


Thus, there is no discrepancies.

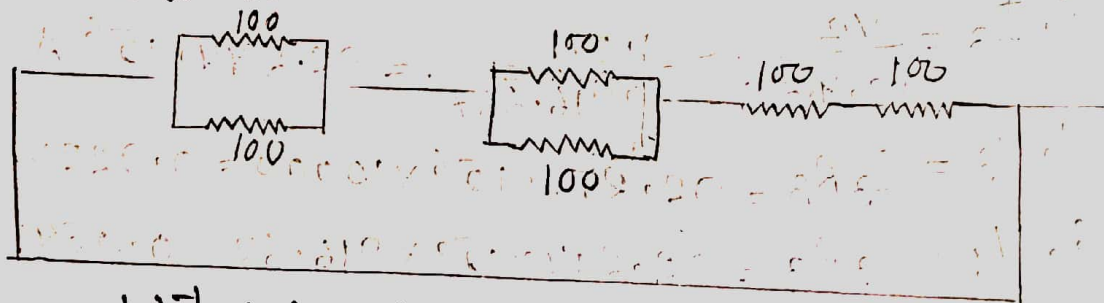2) If we put two 100 ohm parallel resistors then connect with another two 100 ohm parallel resistors and lastly put last two 100 ohm resistors in series, we will get 300 ohm resistance value.



$$\left(\frac{1}{100} + \frac{1}{100}\right)^{-1} + \left(\frac{1}{100} + \frac{1}{100}\right)^{-1} + 100 + 100 = 300 \Omega$$

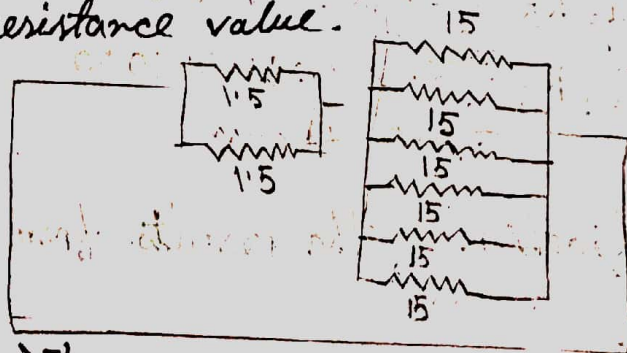3) If we put two parallel 1.5 k ohm resistors then connect it with six parallel 15 k ohm resistors in series, we will get 3.25 k ohm resistance value.



$$\left(\frac{1}{1.5} \times 2\right)^{-1} + \left(\frac{1}{15} + \frac{1}{15} + \frac{1}{15} + \frac{1}{15} + \frac{1}{15} + \frac{1}{15}\right)^{-1} = 3.25$$

Discussion : By comparing voltage and current values we can decide that our experimentation is correct, as the theoretical values and protus file values match each other.

