

# Lab Assignment 03

Name : Ashfia Khanam

ID : 18301231

Section : 09

Course : CSE250

Experiment No : 02

Experiment Name : Verification of KCL and KVL

Signature : Ashfia Khanam




Name of the Experiment: Verification of KCL and KVL.

Objective: KVL This experiment is intended to verify Kirchhoff's voltage law (KVL) with the help of series circuits.

Apparatus:

- ☐ One multimeter
- ☐ One DC Ammeter (0-1A)
- ☐ Three Resistors
- ☐ One DC power supply.

Circuit:

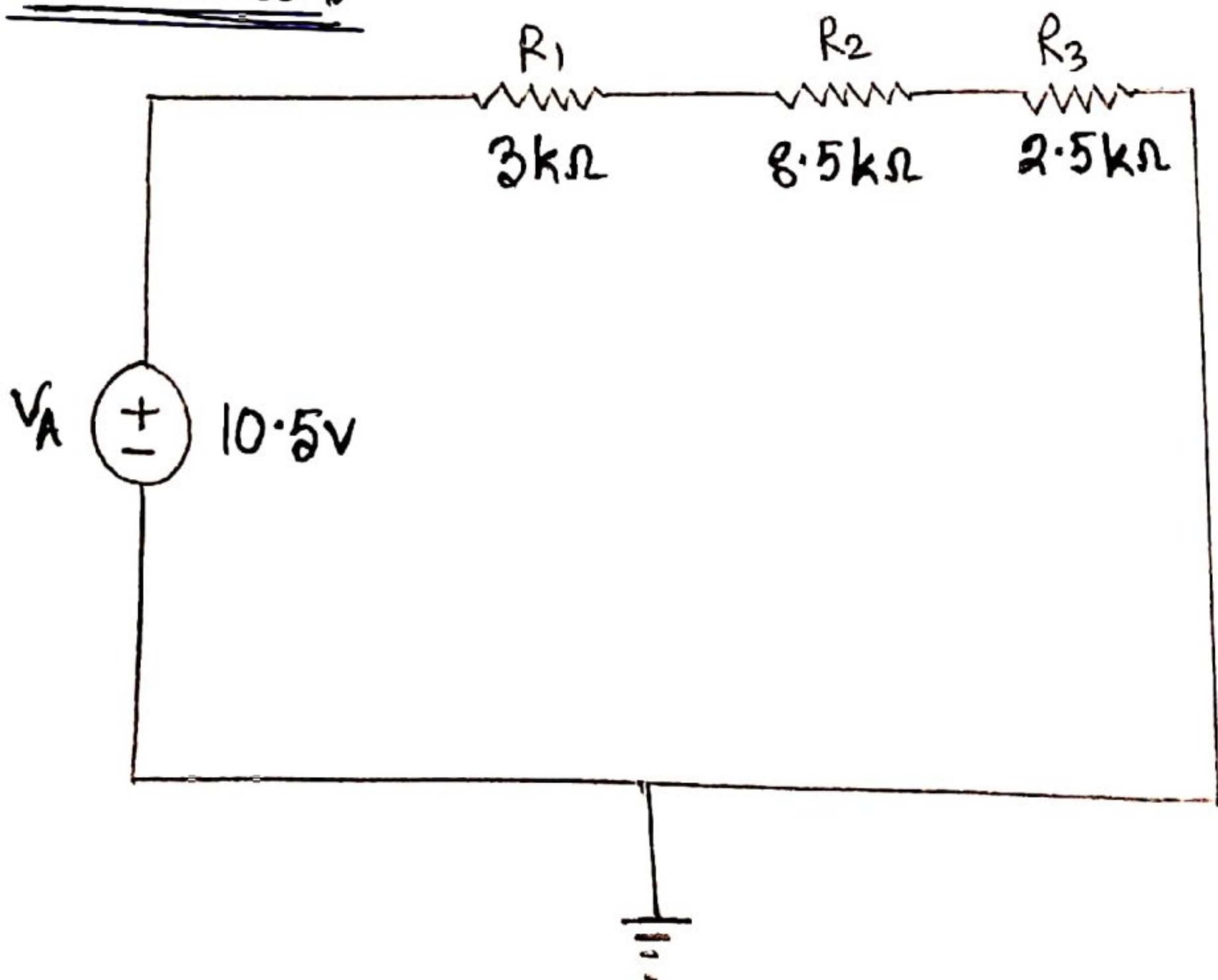



## Analysis:

$$\text{Total resistance, } R = (3.0 + 8.5 + 2.5) \text{ k}\Omega \\ = 14 \text{ k}\Omega$$

$$\text{Current, } I = V/R = 10.5 / 14 \times 10^3 = 0.00075 \text{ A}$$

$$V_1 = 0.00075 \times 3 \times 10^3 = 2.25 \text{ V}$$

$$V_2 = 0.00075 \times 8.5 \times 10^3 = 6.37 \text{ V}$$

$$V_3 = 0.00075 \times 2.5 \times 10^3 = 1.88 \text{ V}$$

$$\therefore V_1 + V_2 + V_3 = (2.25 + 6.37 + 1.88) \text{ V} = 10.5 \text{ V}$$

Table 1: Verification of KVL.

Observation	$R_1$	$R_2$	$R_3$	$V$	$V_1$	$V_2$	$V_3$	$V_1 + V_2 + V_3$
Simulation	3.0	8.5	2.5	10.5	2.25	6.37	1.88	10.5
Theoretical	3.0	8.5	2.5	10.5	2.25	6.37	1.88	10.5

## Report:

- To get ~~more~~ exact value, voltmeter should be connected with the circuit in parallel.
- ~~Since~~ As simulation and theoretical values are same. So, no discrepancies happen. Again, as ~~the~~ source voltage and calculated voltage are same, so the results has matched with KVL theory.

## Discussion:

$V_1 + V_2 + V_3 - V = 0$ , Out of KVL, we find that around any closed circuit; the sum of the algebraic voltage enhances which equivalents with the ~~and~~ sum of algebraic voltage drops. So, KVL Theory proved.




# KCL

Objective : This experiment is intended to verify Kirchhoff's current law (KCL) with the help of a simple parallel circuit.

Apparatus :

- ☐ One DC Ammeter (0-1A)
- ☐ Three Resistors
- ☐ One multimeter
- ☐ One DC supply.

Circuit :

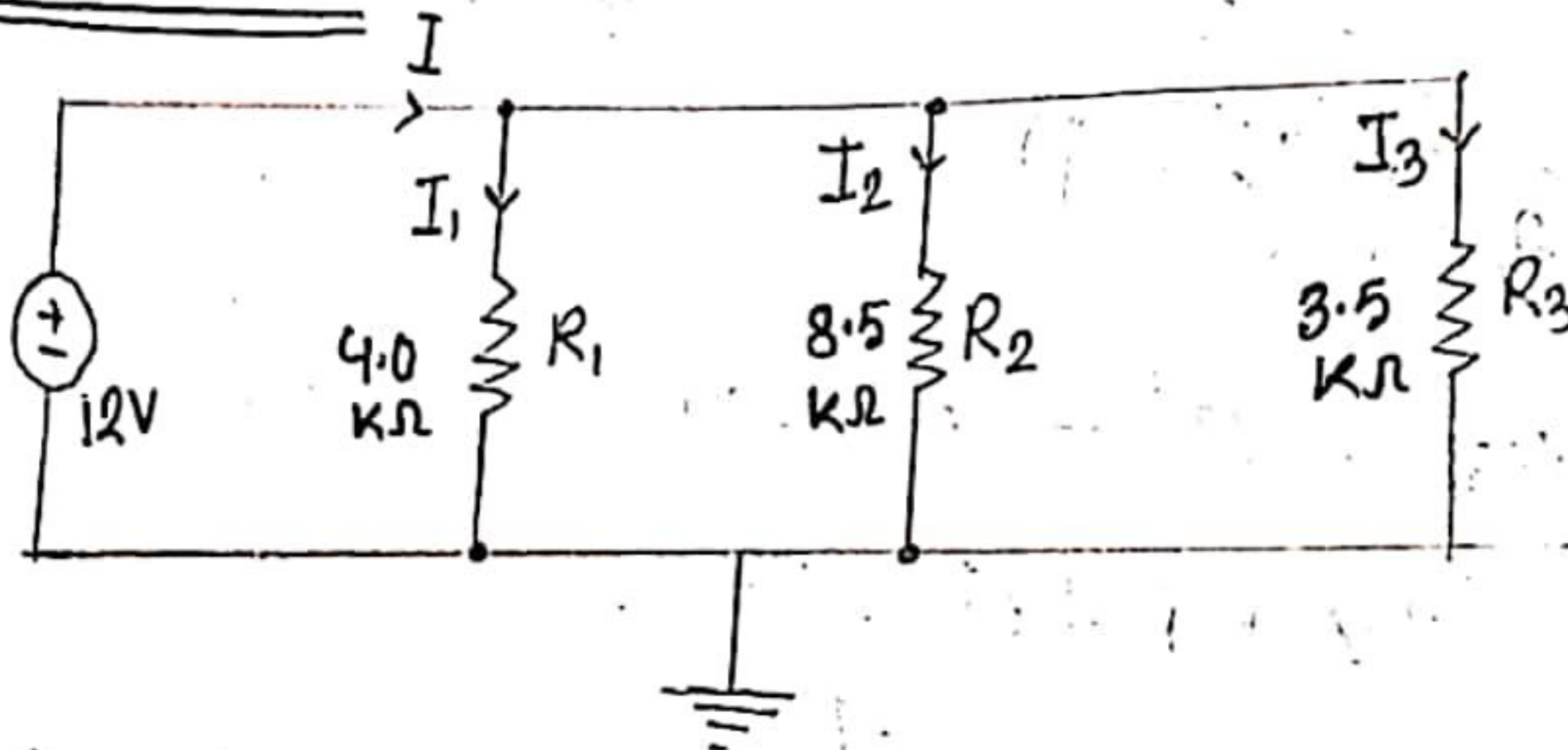

Analysis :

$$I_1 = V/R_1 = 12/4.0 \times 10^3 = 3.00 \text{ mA}$$

$$I_2 = V/R_2 = 12/8.5 \times 10^3 = 1.41 \text{ mA}$$

$$I_3 = V/R_3 = 12/3.5 \times 10^3 = 3.43 \text{ mA}$$

$$\therefore I = I_1 + I_2 + I_3 = (3 + 1.41 + 3.43) \text{ mA} = 7.84 \text{ mA}$$

Table 1 : verification of KCL :

Observation	$R_1$	$R_2$	$R_3$	$I$	$I_1$	$I_2$	$I_3$	$I_1 + I_2 + I_3$
Simulation	4	8.5	3.5	7.84	3.0	1.41	3.43	7.84
Theoretical	4	8.5	3.5	7.84	3.0	1.41	3.43	7.84



## Report:

- ❑ To get the current flows, the ammeter should be connected to ~~the~~ ~~each~~ every resistors and circuits in series.
- ❑ As simulation and theoretical values are same. So no discrepancies happen. Again, as source current and calculated current values are same. So, the results has matched with KCL theory.

Discussion:  $I_1 + I_2 + I_3 - I = 0$ , out of KCL, we find the ~~sum~~ sum of algebraic of the currents entering to any node ~~is~~ equivalent with the sum of current leaving node. So, KCL proved.



