

LAB Assignment : 04

Name : Ashfia Khanam

ID : 18301231

Course : CSE250

Section : 09

Signature : Ashfia Khanam

Experiment no : 03

Experiment name : Verification of superposition principle.


Experiment. No : 03

Name of the Experiment : Verification of Superposition principle.


Objective : The experiment is to verify experimentally the Superposition theorem which is an analytical technique of determining currents in a circuit with more than one emf source.




Circuit Diagram :




Circuit 01 :

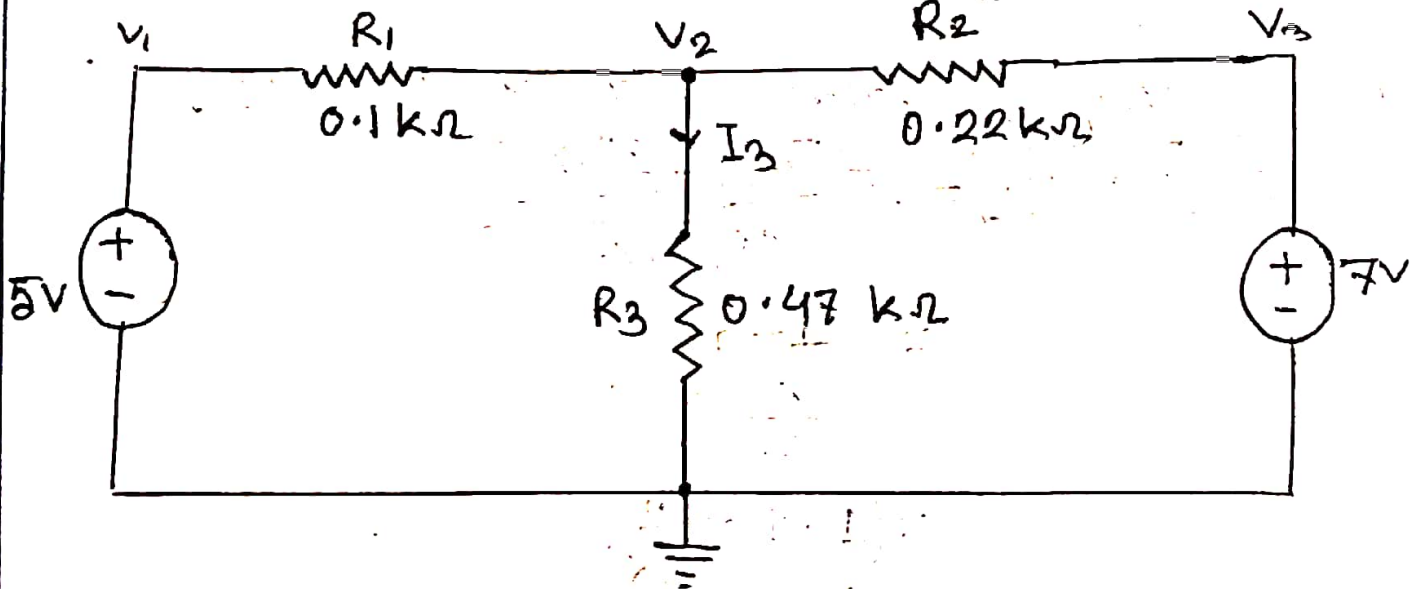

Circuit 02 :

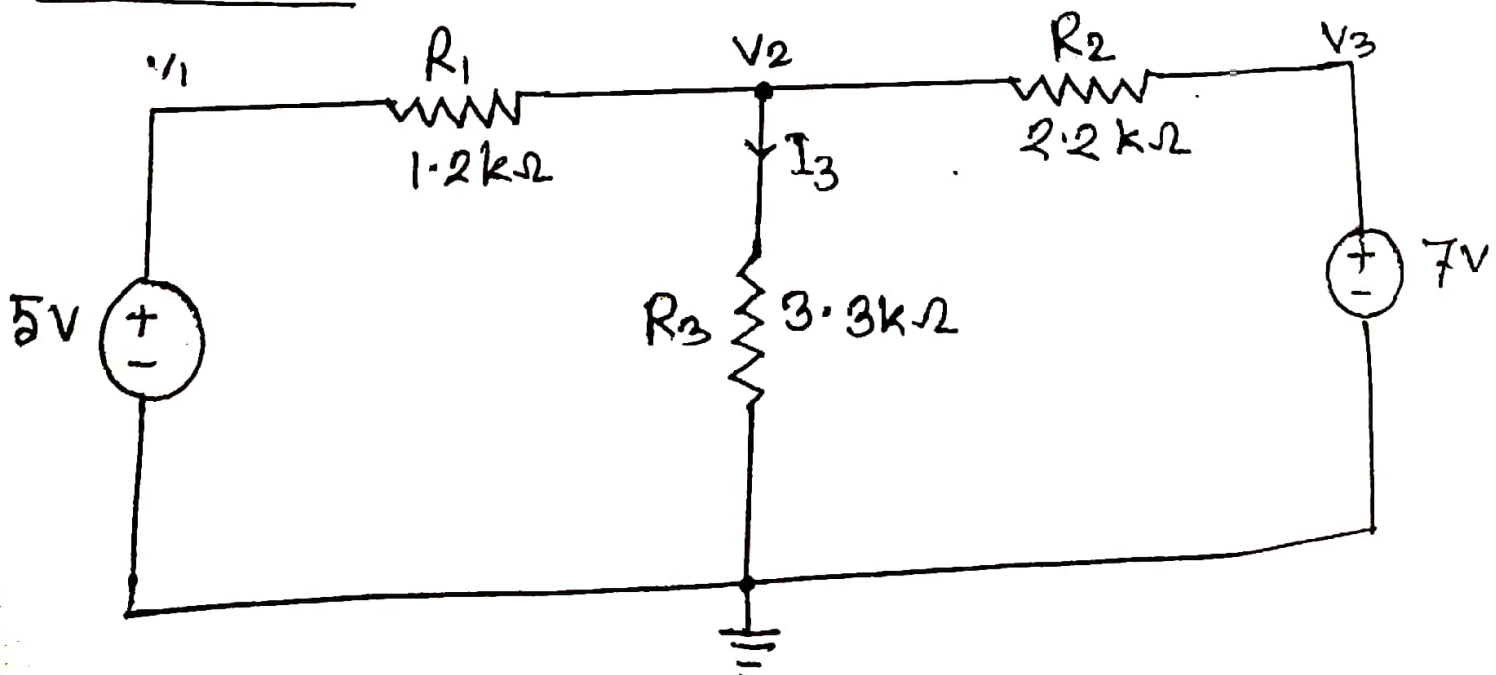

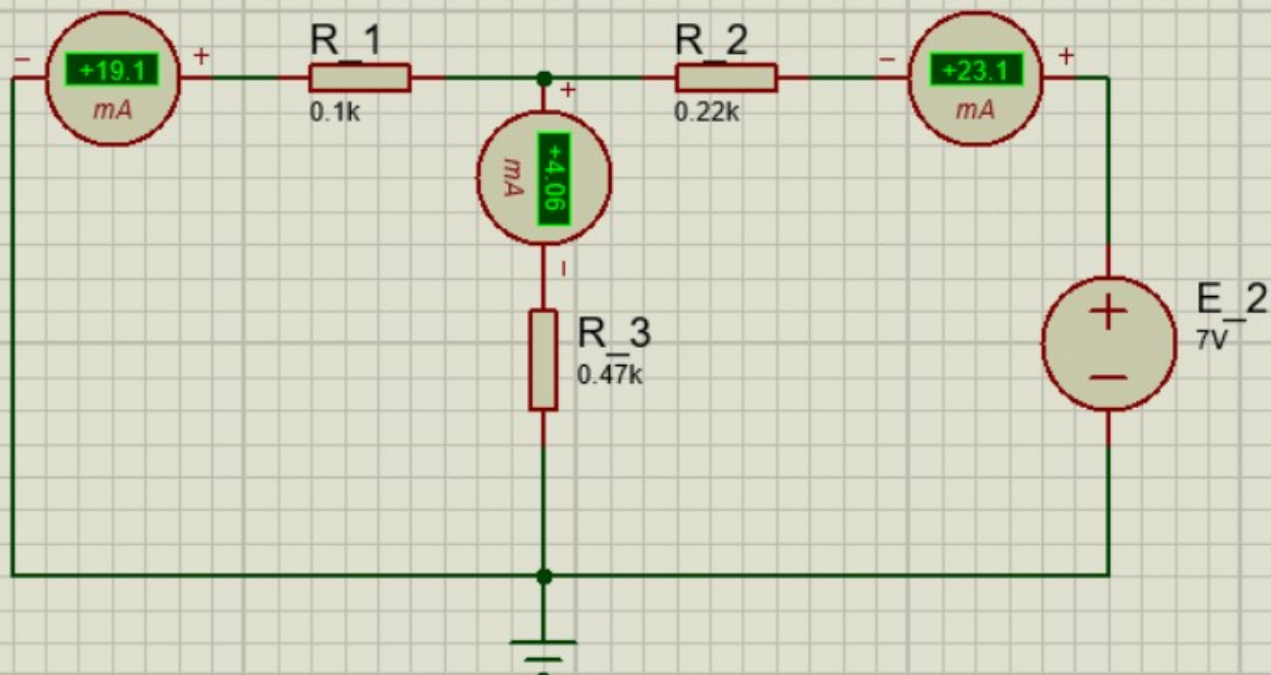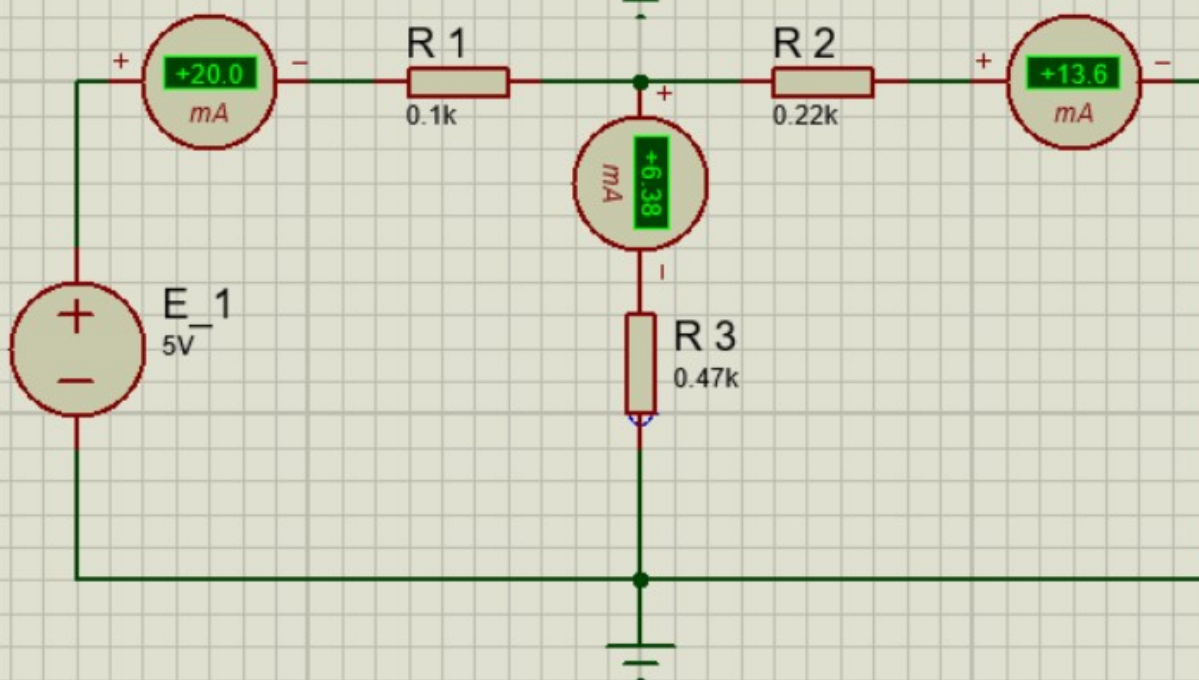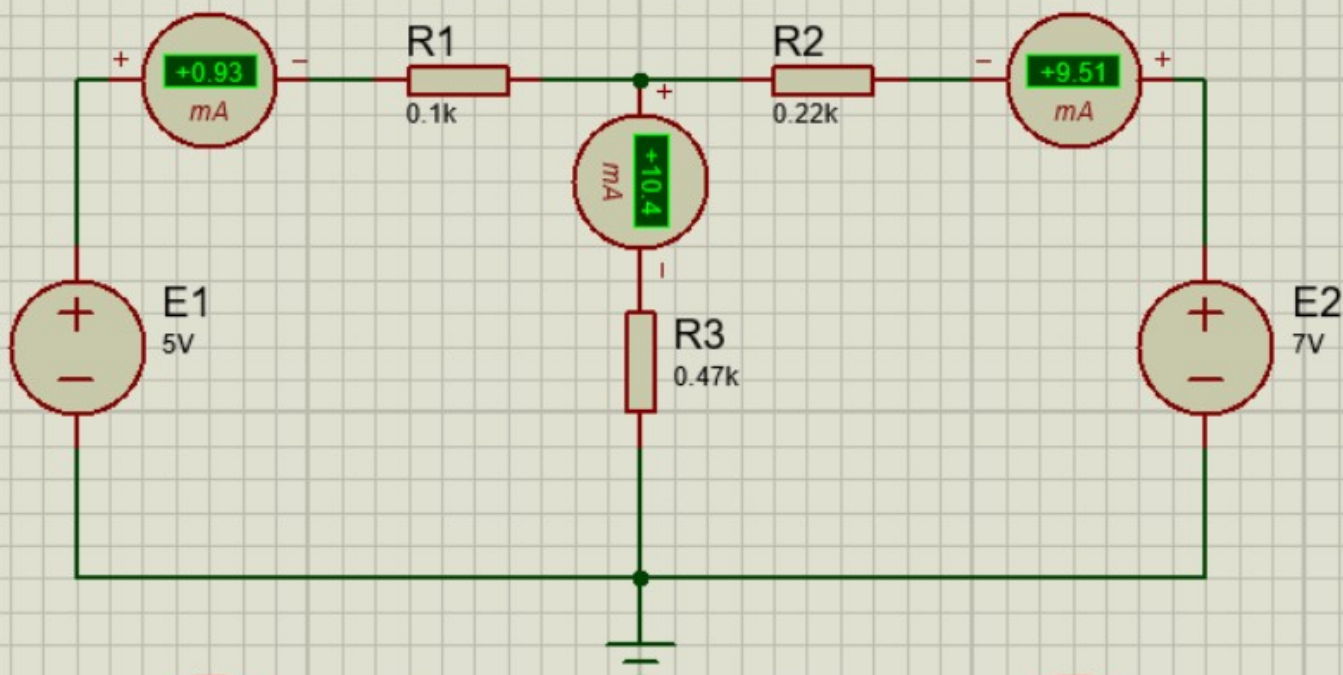

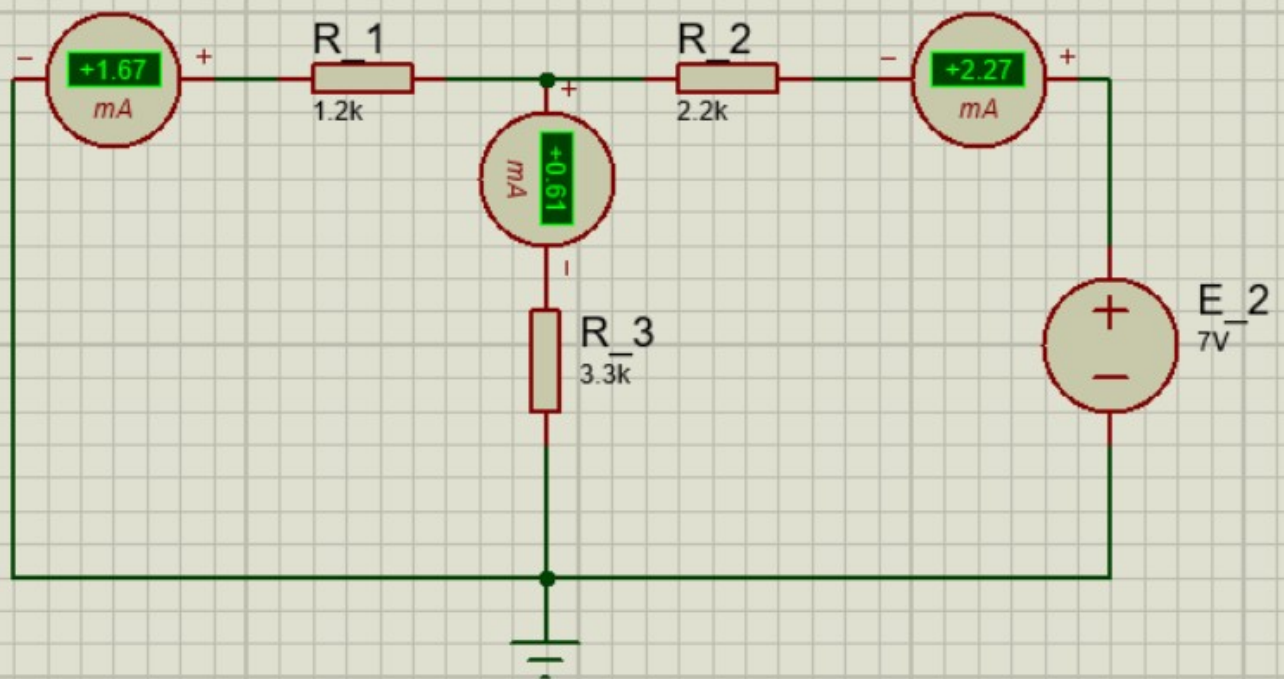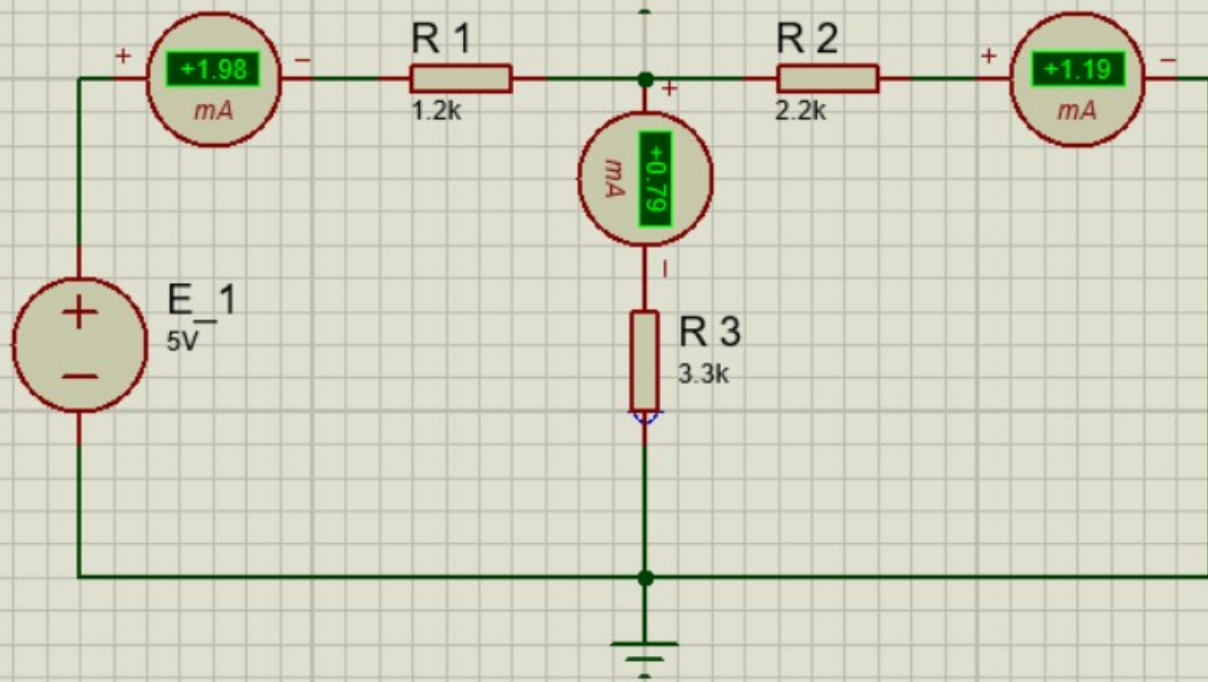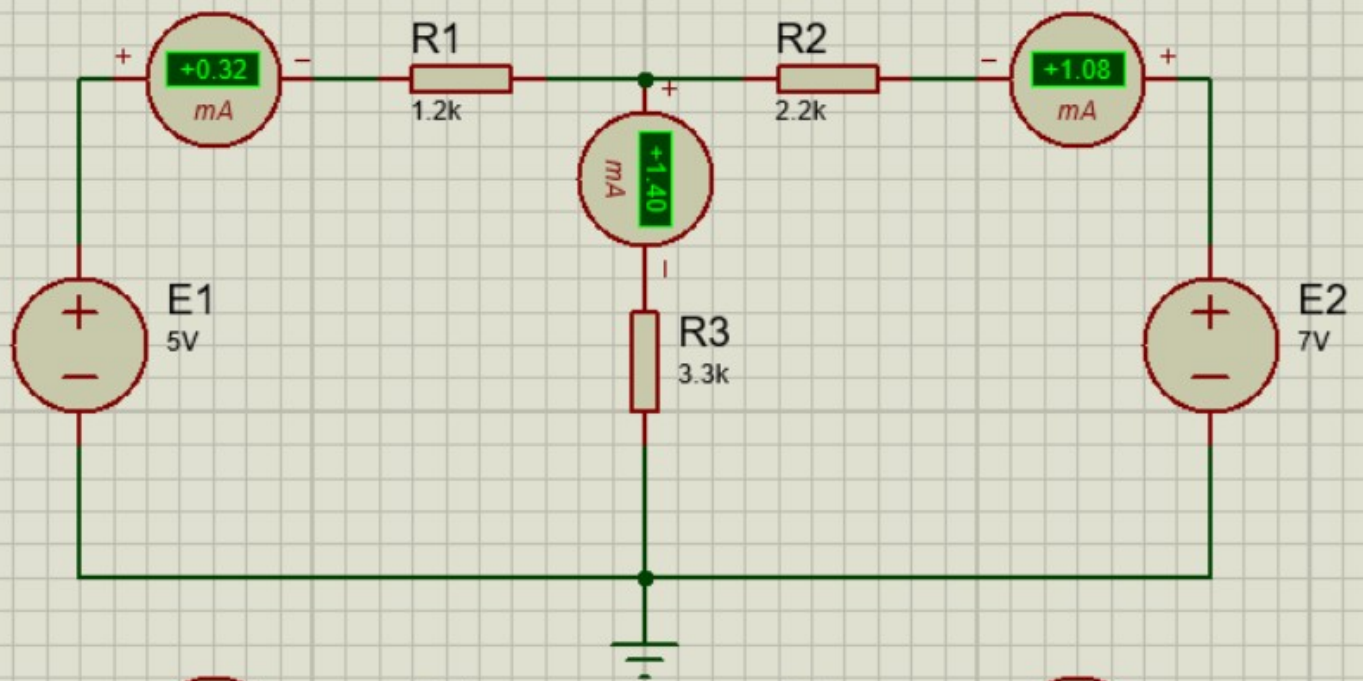

Result/Analysis:

Circuit 01: when $E_1 = 5V$ and $E_2 = 7V$

$$V_1 = 5$$

$$V_2 = 7$$

$$\text{Also, } R_1 = 0.1 k\Omega = 100 \Omega ; R_2 = 0.22 k\Omega = 220 \Omega$$

$$\text{Now, } R_3 = 0.47 k\Omega = 470 \Omega$$

$$V_2 \left(\frac{1}{100} + \frac{1}{220} + \frac{1}{470} \right) - \frac{5}{100} - \frac{7}{220} = 0$$

$$\Rightarrow 0.0167V_2 - 0.0818 = 0$$

$$\Rightarrow V_2 = 4.907V$$

$$\text{So, } I_3 = \frac{V_2 - 0}{R_3} = \frac{4.907}{470} = 0.0104A = 10.4 \text{ mA}$$

$$\text{When, } E_1 = 5V \text{ but } E_2 = 0V,$$

$$V_1 = 5.$$

$$\text{Now, } V_2 \left(\frac{1}{100} + \frac{1}{220} + \frac{1}{470} \right) - \frac{5}{100} = 0$$

$$\Rightarrow 0.01667V_2 - 0.05 = 0$$

$$\Rightarrow V_2 = 2.998V.$$

$$\text{So, } I'_3 = \frac{V_2 - 0}{R_3} = \frac{2.998}{470} = 6.38 \text{ mA}$$

$$\text{When } E_1 = 0V ; E_2 = 7V ; V_3 = 7$$

$$V_2 \left(\frac{1}{100} + \frac{1}{220} + \frac{1}{470} \right) - \frac{7}{100} = 0$$

$$\Rightarrow 1.667V_2 - 0.0318 = 0$$

$$\Rightarrow V_2 = 1.908V$$

$$\text{So, } I''_3 = \frac{V_2 - 0}{R_3} = \frac{1.908}{470} = 4.060 \text{ mA}$$

Table for circuit 01:

Observation	R_1 (k Ω)	R_2 (k Ω)	R_3 (k Ω)	I_3' (mA)	I_3'' (mA)	$I_3' + I_3''$ (mA)	I_3 (mA)
Simulation	0.1	0.22	0.47	6.38	4.06	10.44	10.4
Theoretical	0.1	0.22	0.47	6.38	4.06	10.44	10.4

So, the theoretical results and the simulation results are ~~var~~ verified.

Circuit 2:

when $E_1 = 5V$ and $E_2 = 7V$

$$V_1 = 5; V_3 = 7$$

$$R_1 = 1.2 k\Omega = 1200\Omega; R_2 = 2.2 k\Omega = 2200\Omega$$

$$\text{Now, } R_3 = 3.3 k\Omega = 3300\Omega$$

$$V_2 \left(\frac{1}{1200} + \frac{1}{2200} + \frac{1}{3300} \right) - \frac{5}{1200} - \frac{7}{2200} = 0$$

$$\Rightarrow 0.00159V_2 - 0.00416 - 0.00318 = 0$$

$$\Rightarrow V_2 = 4.617V$$

$$\therefore I_3 = \frac{V_2 - 0}{R_3} = \frac{4.617}{3300} = 0.001398A = 1.40mA$$

when, $E_1 = 5V$ but $E_2 = 0V$

$$V_1 = 5$$

Now,

$$V_2 \left(\frac{1}{1200} + \frac{1}{2200} + \frac{1}{3300} \right) - \frac{5}{1200} = 0$$

$$\Rightarrow 0.00159V_2 - 0.00416 = 0$$

$$\Rightarrow V_2 = 2.616V$$

$$\therefore I_3' = \frac{V_2 - 0}{R_3} = \frac{2.616}{3300} = 0.000792A = 0.79mA$$

when, $E_1 = 0V$ but $E_2 = 7V$

$$V_3 = 7$$

Now,

$$V_2 \left(\frac{1}{1200} + \frac{1}{2200} + \frac{1}{3300} \right) - \frac{7}{2200} = 0$$

$$\Rightarrow 0.00159 V_2 - 0.00318 = 0$$

$$\Rightarrow V_2 = 2V$$

$$\therefore I_3'' = \frac{V_2 + 0}{R_3} = \frac{2}{3300} = 0.000606A = 0.61mA$$

Table for circuit-2:

Observation	R_1 ($k\Omega$)	R_2 ($k\Omega$)	R_3 ($k\Omega$)	I_3 (mA)	I_3' (mA)	$I_3' + I_3''$ (mA)	I_3 (mA)
Simulation	1.2	2.2	3.3	0.79	0.60	1.4	1.40
Theoretical	1.2	2.2	3.3	0.79	0.61	1.4	1.40

So, the theoretical results and the simulation results are verified.

Question - answer:

□ Linear Element : A linear relationship between voltage and current.

□ Linear circuit : A linear circuit is one in which the electronic components values, such as resistance, capacitance, inductance, gain etc. are constant even in different voltage and current.

□ ~~Linear~~ Nonlinear Element : A nonlinear relationship between voltage and current.

□ Nonlinear circuit : A nonlinear circuit is one in which the electronic components values such as resistance, capacitance, inductance, gain etc. changes for different voltage and current.

(2) we know,

$$P = I^2 R$$

$$\Rightarrow P = \frac{V^2}{R}$$

and,

$$V = IR$$

$$\Rightarrow I = \frac{V}{R}$$

It will give wrong result for a superposition principle because the equation of power is quadratic.

— 0 —

(3) By short circuiting, the independent voltage source deactivated and by open circuit independent current source deactivated.

Reasons are : Independent ~~and~~ voltage circuit acts like a single node on the other hand independent current source acts like ~~the~~ no nodes there.
~~that that mean~~

Those indicates that in independent voltage source no voltage difference will show.

On contrary, in independent current source no current will flow.

④ From results and analysis part, we get,

$$I = 10.4 \text{ mA}$$

[in circuit 0]

and,

$$I = 1.40 \text{ mA}$$

[in circuit 2]

Discussion:

The results are the same of ~~experiment~~ theoretical and simulation.

So, we can say that the theoretical part is correct. (prove).

~~So~~ There is no error in the experiment. So, the result should be corrected.